

## 1.14 Differentiators

Look at the circuit in Figure 1.34. The voltage across  $C$  is  $V_{\text{in}} - V$ , so

$$I = C \frac{d}{dt} (V_{\text{in}} - V) = \frac{V}{R}$$

If we choose  $R$  and  $C$  small enough so that  $dV/dt \ll dV_{\text{in}}/dt$ , then

$$C \frac{dV_{\text{in}}}{dt} \approx \frac{V}{R}$$

or

$$V(t) = RC \frac{d}{dt} V_{\text{in}}(t)$$

That is, we get an output proportional to the rate of change of the input waveform.

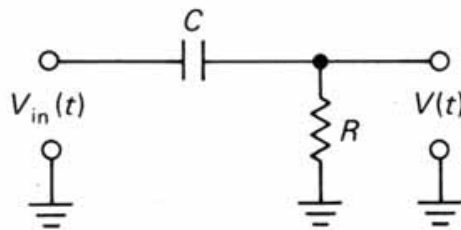


Figure 1.34

To keep  $dV/dt \ll dV_{\text{in}}/dt$ , we make the product  $RC$  small, taking care not to "load" the input by making  $R$  too small (at the transition the change in voltage across the

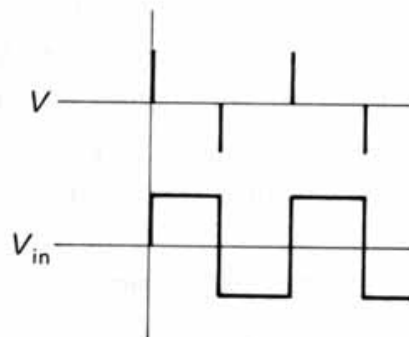


Figure 1.35

capacitor is zero, so  $R$  is the load seen by the input). We will have a better criterion for this when we look at things in the frequency domain. If you drive this circuit with a square wave, the output will be as shown in Figure 1.35.

Differentiators are handy for detecting *leading edges* and *trailing edges* in pulse signals, and in digital circuitry you sometimes see things like those depicted in Figure 1.36. The  $RC$  differentiator generates spikes

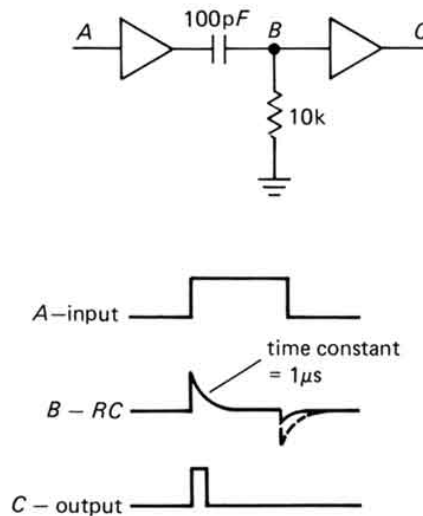


Figure 1.36

at the transitions of the input signal, and the output buffer converts the spikes to short square-topped pulses. In practice, the negative spike will be small because of a diode (a handy device discussed in Section 1.25) built into the buffer.

### **Unintentional capacitive coupling**

Differentiators sometimes crop up unexpectedly, in situations where they're not welcome. You may see signals like those shown in Figure 1.37. The first case is caused by a square wave somewhere in the circuit coupling capacitively to the signal line you're looking at; that might indicate a miss-

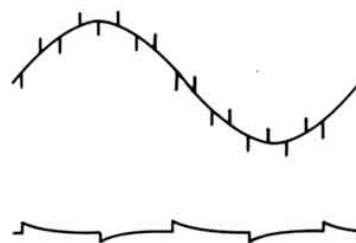


Figure 1.37

ing resistor termination on your signal line. If not, you must either reduce the source resistance of the signal line or find a way to reduce capacitive coupling from the offending square wave. The second case is typical of what you might see when you look at a square wave, but have a broken connection somewhere, usually at the scope probe. The very small capacitance of the broken connection combines with the scope input resistance to form a differentiator. *Knowing that you've got a differentiated "something" can help you find the trouble and eliminate it.*

### 1.15 Integrators

Take a look at the circuit in Figure 1.38. The voltage across  $R$  is  $V_{in} - V$ , so

$$I = C \frac{dV}{dt} = \frac{V_{in} - V}{R}$$

If we manage to keep  $V \ll V_{in}$ , by keeping the product  $RC$  large, then

$$C \frac{dV}{dt} \approx \frac{V_{in}}{R}$$

or

$$V(t) = \frac{1}{RC} \int^t V_{in}(t) dt + \text{constant}$$

We have a circuit that performs the integral over time of an input signal! You can see how the approximation works for a square-wave input:  $V(t)$  is then the exponential

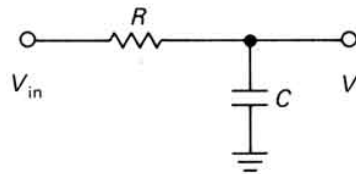


Figure 1.38

charging curve we saw earlier (Fig. 1.39). The first part of the exponential is a ramp, the integral of a constant; as we increase the time constant  $RC$ , we pick off a smaller part of the exponential, i.e., a better approximation to a perfect ramp.

Note that the condition  $V \ll V_{in}$  is just the same as saying that  $I$  is proportional to  $V_{in}$ . If we had as input a *current*  $I(t)$ , rather than a

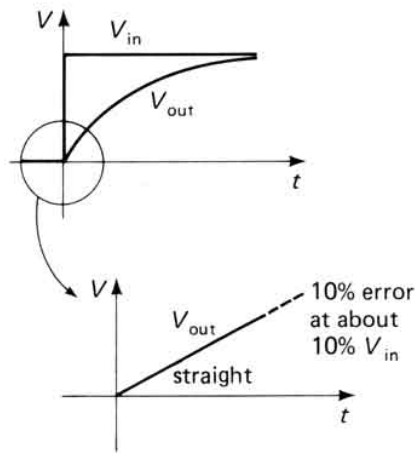


Figure 1.39

voltage, we would have an exact integrator. A large voltage across a large resistance approximates a current source and, in fact, is frequently used as one.

Later, when we get to operational amplifiers and feedback, we will be able to build integrators without the restriction  $V_{out} \ll V_{in}$ . They will work over large frequency and voltage ranges with negligible error.

The integrator is used extensively in analog computation. It is a useful subcircuit that finds application in control systems, feedback, analog/digital conversion, and waveform generation.

### ***Ramp generators***

At this point it is easy to understand how a ramp generator works. This nice circuit is extremely useful, for example in timing circuits, waveform and function generators, oscilloscope sweep circuits, and analog/digital conversion circuitry. The circuit is shown in Figure 1.40. From the capacitor equation

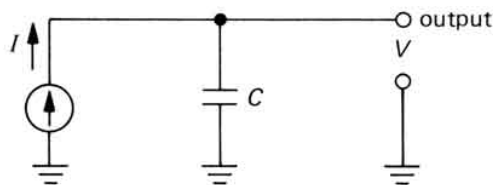


Figure 1.40

$I = C(dV/dt)$ , you get  $V(t) = (I/C)t$ . The output waveform is as shown in Figure 1.41. The ramp stops when the current source "runs out of voltage," i.e., reaches the limit of its compliance. The curve for a simple  $RC$ , with the resistor tied to a voltage source equal to the compliance of the current source, and with  $R$  chosen so that